


Project Report

Temperature Monitoring and Alarm System

Amaim Anwar 23i-2614

Dania Waseem 23i-2622

Munaza Tariq 23i-2545

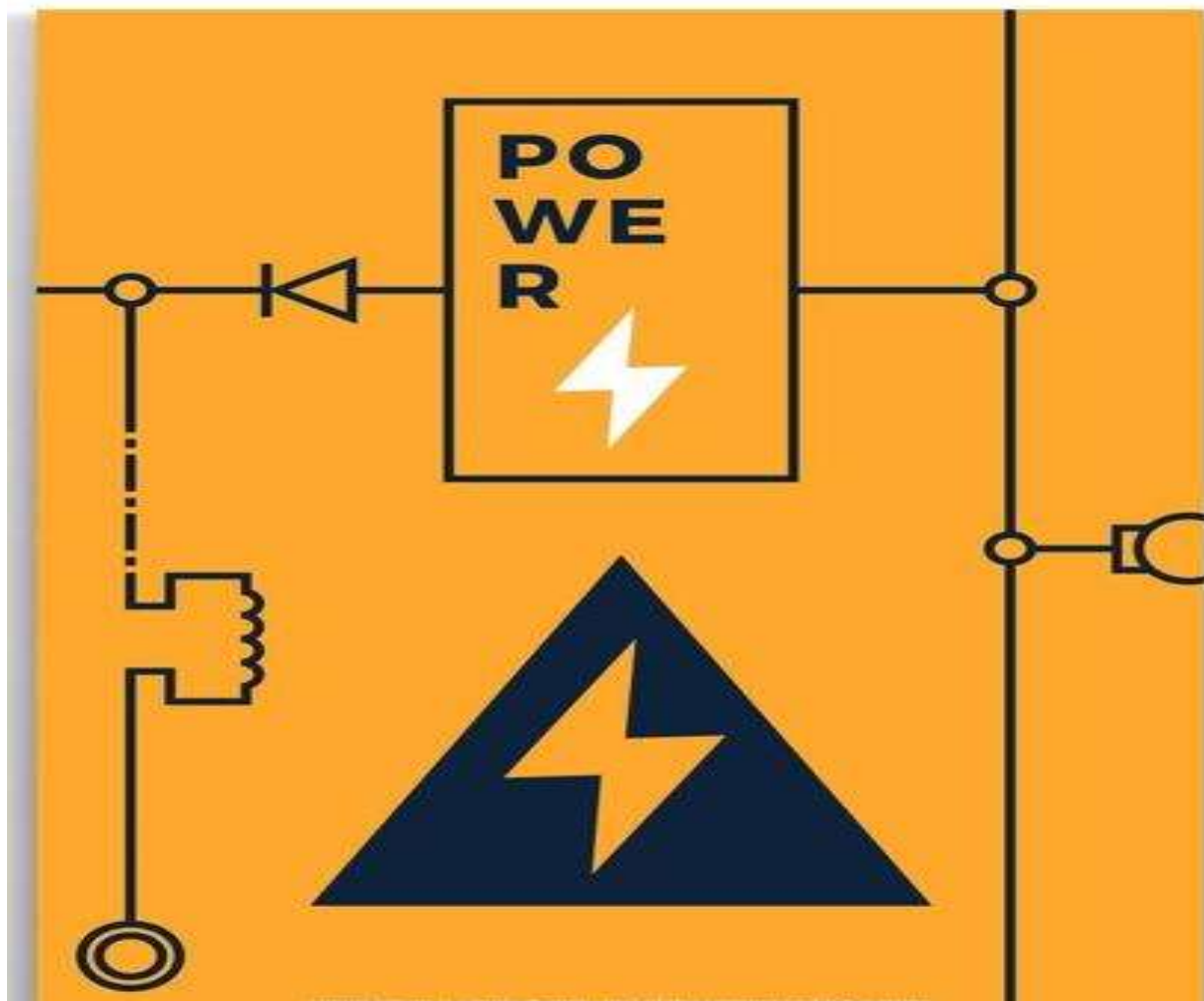

Project Summary

Objective: This project aims to design and implement a **Temperature Monitoring and Alarm System**. The system monitors ambient temperature using an LM35 temperature sensor, displays the current temperature on a seven-segment display, and activates visual and audio indicators based on pre-defined thresholds. This project is significant in environments requiring real-time temperature monitoring to prevent overheating or other temperature-related hazards.

Significance:

The system ensures safety by indicating:

1. **Safe Temperature Range:** A green LED lights up.
2. **Near-Threshold Alert:** A yellow LED activates when temperatures are near the set limit.
3. **High-Temperature Alarm:** A red LED lights up with a buzzer to signal dangerous temperatures.

Significance of the Circuit in Real Life

This circuit has practical applications in various real-life scenarios, ensuring safety and efficiency in environments where temperature monitoring is critical. For instance:

1. **Industrial Settings:** Prevents overheating of machinery or equipment by providing early alerts.
2. **Healthcare Applications:** Ensures safe temperature conditions for sensitive medical equipment or storage of vaccines.

3. **Data Centers:** Prevents server overheating by activating alarms for unsafe conditions.

This system ensures timely responses to temperature deviations, protecting both equipment and human lives.

Functionality:

1. The LM35 sensor reads the temperature.
2. The data is processed by a comparator-based logic circuit and displayed on a seven-segment display.
3. Based on the thresholds:
 - a. **Green LED** lights up for safe temperature.
 - b. **Yellow LED** warns of approaching limits.
 - c. **Red LED and buzzer** activate for dangerous temperatures.

Components List

Software used: Proteus (for circuit simulation)

Component	Quantity	Description
LM35	1	Temperature sensor
TC7107	1	ADC for seven-segment display driver
Seven-Segment Display (common anode)	3	Displays temperature in °C
741 (Op-Amp)	6	Operational amplifiers as comparators
Potentiometers (RV1-RV6)	6	Adjustable temperature thresholds
LEDs (Green,Yellow,Red)	3	Visual indicators
Buzzer	1	Audio indicator for high temperature
Resistors	Multiple	For current limiting and pull-down

Capacitors	Multiple	Stabilization and filtering
AND	3 gates	Ensures only the correct LED or buzzer is activated for each range.
NOT	3 gates	Inverts comparator outputs to manage LED/buzzer activation logic.
Power Supply (Battery)	1	Provides power to the circuit

Implementation Details

Circuit Design and Logic

The circuit consists of the following modules:

- 1. Temperature Sensor (LM35):**
 - a. Outputs a voltage proportional to the temperature (10mV/°C).
 - b. Connected to the inputs of a voltage comparator for processing.
- 2. Comparator Circuit:**
 - a. Adjustable thresholds set using potentiometers (RV1 to RV6).
 - b. Comparators (U3, U4, U7, U8, U11, U12) determine whether the current temperature is below, near, or above the threshold values.
- 3. Display Logic:**
 - a. The output of the LM35 is sent to the TC7107 IC, which converts the analog input into a digital signal and drives a **three-digit seven-segment display**.
- 4. Indicator LEDs and Buzzer:**
 - a. Logic gates (NOT and AND) process the comparator outputs to control LEDs (green, yellow, red) and the buzzer.

Thresholds

LED	Thresholds (degree Celsius)
Green	1 to 49
Yellow	50 to 99
Red + Buzzer	100 to 149

Logic Function for Safe Range (Green LED):

- Input Conditions: Temp < Lower Threshold
- Truth Table:

Temp	Output (D1 - Green)
$< T1$	1 (ON)
$\geq T1$	0 (OFF)

Logic Function for Near-Threshold (Yellow LED):

- Input Conditions: $T1 \leq \text{Temp} < T2$
- Truth Table:

Temp Range	Output (D2 - Yellow)
$< T1$	0 (OFF)
$T1 \text{ to } T2$	1 (ON)
$> T2$	0 (OFF)

Logic Function for Dangerous Temperature (Red LED + Buzzer):

- Input Conditions: $\text{Temp} > \text{Upper Threshold}$
- Truth Table:

Temp	Output (D3 - Red, Buzzer)
$\leq T2$	0 (OFF)
$> T2$	1 (ON)

1. Circuit Overview

The circuit is divided into the following functional sections:

- **Temperature Sensing**
- **Comparator Logic**
- **Indicator System (LEDs and Buzzer)**
- **Seven-Segment Display**

2. Temperature Sensing with LM35

- **Component Function:**
 - The LM35 sensor outputs a voltage proportional to the ambient temperature, at a rate of **10mV per °C**. For example:
 - $25^{\circ}\text{C} \rightarrow 250\text{mV}$
 - $50^{\circ}\text{C} \rightarrow 500\text{mV}$

- $100^{\circ}\text{C} \rightarrow 1000\text{mV (1V)}$
- **Circuit Operation:**
 - The LM35 is powered with a 5V DC supply.
 - Its output voltage is fed into a **buffer circuit** (usually an operational amplifier like 741 in a unity gain configuration) to stabilize the signal and prevent loading effects.
 - The buffered output is then sent to:
 - **Comparator circuit** for range classification.
 - **ADC (Analog-to-Digital Converter)** in the display driver for temperature display.

3. Comparator Logic (741 IC)

- **Purpose:**
 - The comparator circuit compares the LM35's output voltage against predefined thresholds (set by potentiometers) to classify the temperature into ranges:
- **Component Details:**
 - **741 Operational Amplifier:**
 - Each 741 IC is configured as a voltage comparator.
 - The **inverting input (-)** receives the voltage from the LM35.
 - The **non-inverting input (+)** is connected to a reference voltage set by a potentiometer (RV1, RV2, etc.).
 - **Potentiometers (RV1, RV2, RV3):**
 - These are variable resistors used to adjust the reference voltage for the comparators.
 - For example:
 - RV1 sets the threshold for 50°C .
 - RV2 sets the threshold for 100°C .
 - **Comparator Output:**
 - When the LM35 output voltage exceeds the reference voltage, the comparator's output goes high, triggering the corresponding LED or buzzer.
 - Logic gates (NOT, AND) are used to ensure that only one indicator (green, yellow, or red + buzzer) is active at a time.

4. Indicator System (LEDs and Buzzer)

- **Green LED:**
 - Connected to the output of the first comparator.
- **Yellow LED:**

- Connected to the output of the second comparator
- **Red LED and Buzzer:**
 - The red LED and buzzer are connected to the output of the third comparator
 - A NOT gate ensures the buzzer is off when the red LED is inactive.
- **Logic Circuit:**
 - **NOT Gate:**
 - Inverts the output of one comparator to drive another device
 - **AND Gate:**
 - Combines comparator outputs to prevent conflicting signals

5. Temperature Display on Seven-Segment Display

- **Component:**
 - A **TC7107 IC** is used as an ADC and display driver.
 - It converts the analog voltage from the LM35 into a digital output for the seven-segment display.
- **Circuit Operation:**
 - The LM35's output is scaled to match the ADC's input range (typically 0–2V).
 - The TC7107 processes this signal and drives a **three-digit seven-segment display**, showing the temperature in °C.
 - Example:
 - 25°C → "025"
 - 75°C → "075"
 - 110°C → "110"
- **Display Calibration:**
 - The reference voltage for the TC7107 is set using a precision resistor or potentiometer.
 - This ensures accurate conversion of the LM35's output voltage to the displayed value.

Comparator Logic

- V_{in} (from LM35): T (temperature in °C, scaled as 10 mV/°C).
- V_{ref} (set by potentiometer): Adjustable threshold voltage.

The comparator output depends on the relationship between V_{in} and V_{ref} :

V_{in}	V_{ref}	Comparator Output
LOW (0°C–49°C)	LOW (50°C threshold)	0

HIGH (50°C–100°C)	LOW (50°C threshold)	1
HIGH (>100°C)	HIGH (>100°C)	1
LOW (<100°C)	HIGH (>100°C)	0

K-Map for Comparator Output

We treat V_{in} and V_{ref} as binary conditions for simplicity (LOW = 0, HIGH = 1).

$V_{in} \backslash V_{ref}$	0	1
0 (LOW)	0	0
1 (HIGH)	1	1


$O = V_{in}$

This indicates the output is HIGH when $V_{in} > V_{ref}$


Circuit Design

(due to the circuit being large it is pasted in parts for better understanding)


Displaying LM35 Temperature

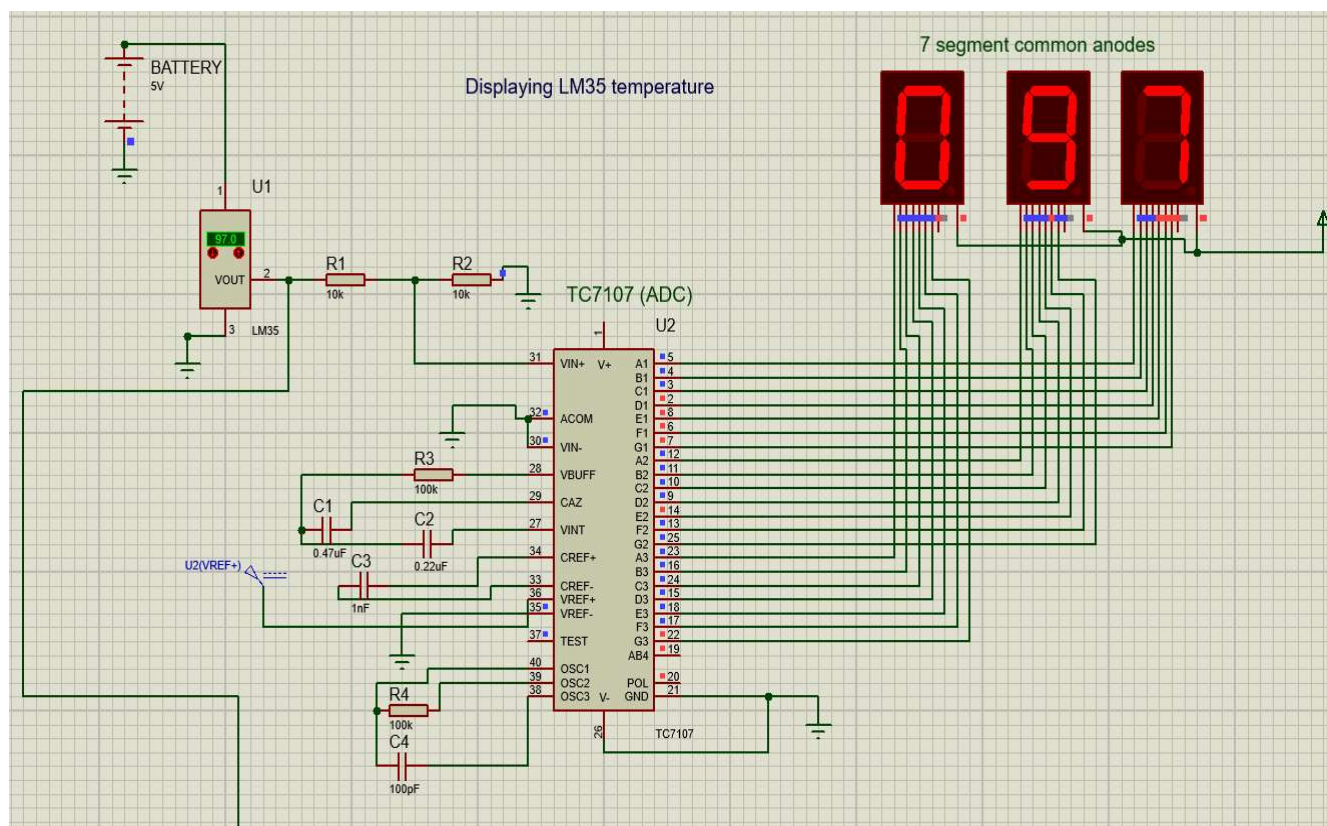

Green LED Part

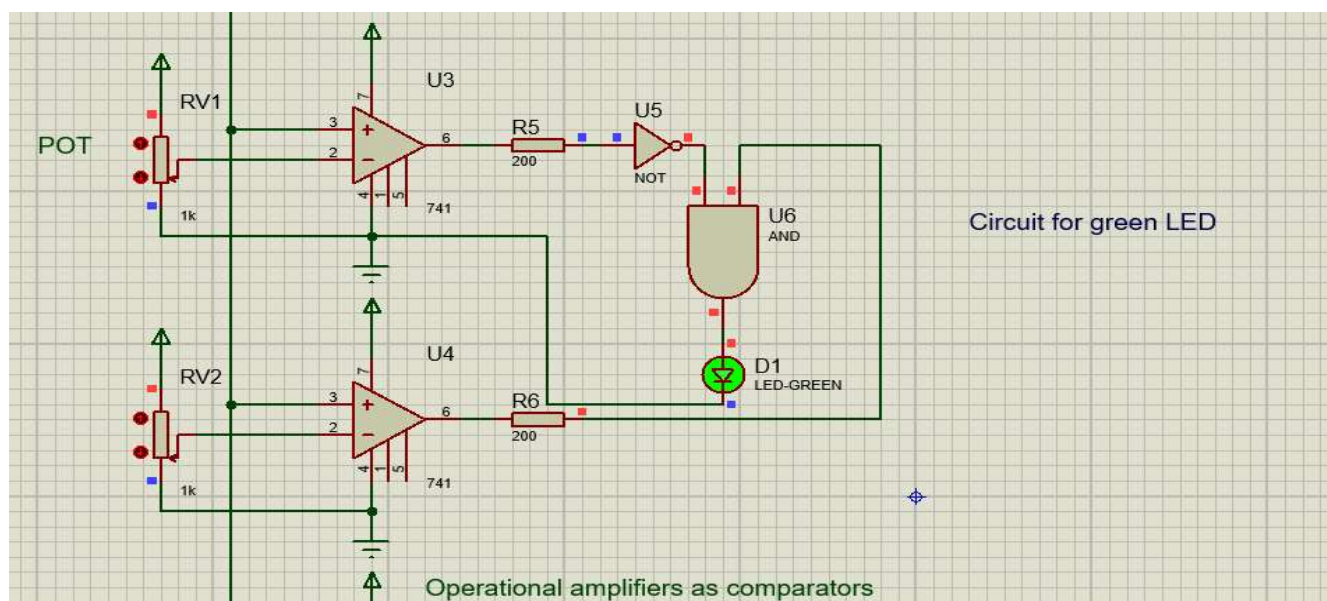

Yellow LED Part

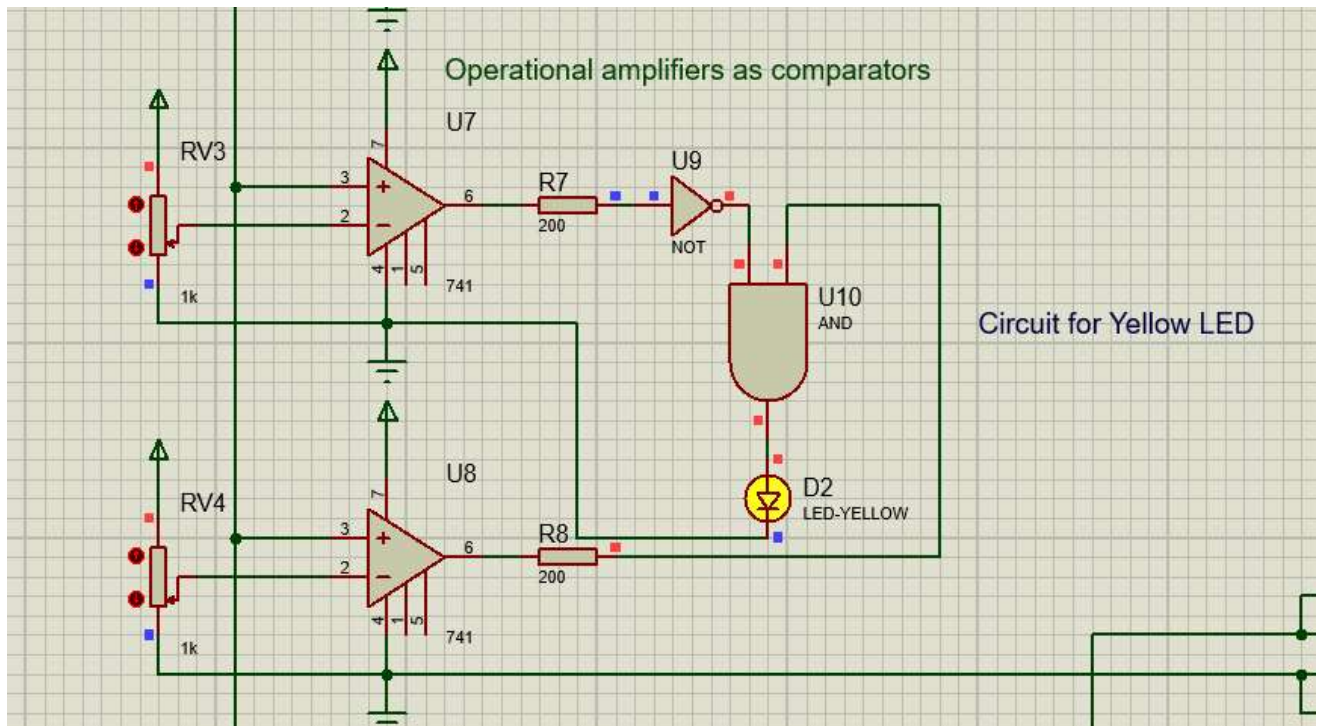

Red LED and Buzzer

